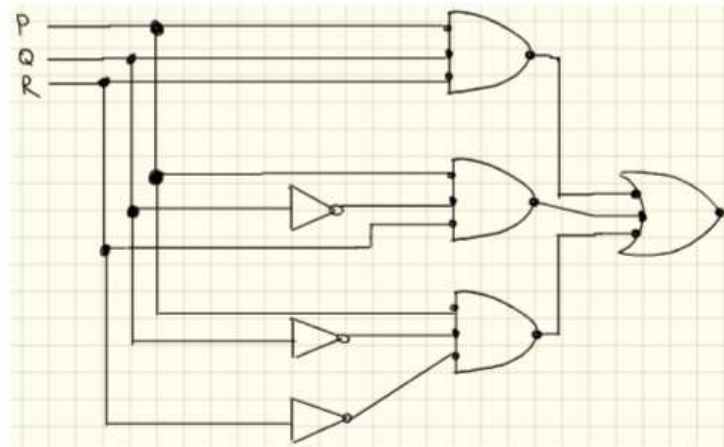



IX.2. For the circuit given below



- What is the output signal for the input signals $P = 0, Q = 1, R = 1$?
- What logical formula in Disjunctive Normal Form (DNF) describes the behaviour of the circuit?
- Use equivalence laws to simplify the formula from item (b).

Solution:

(a):

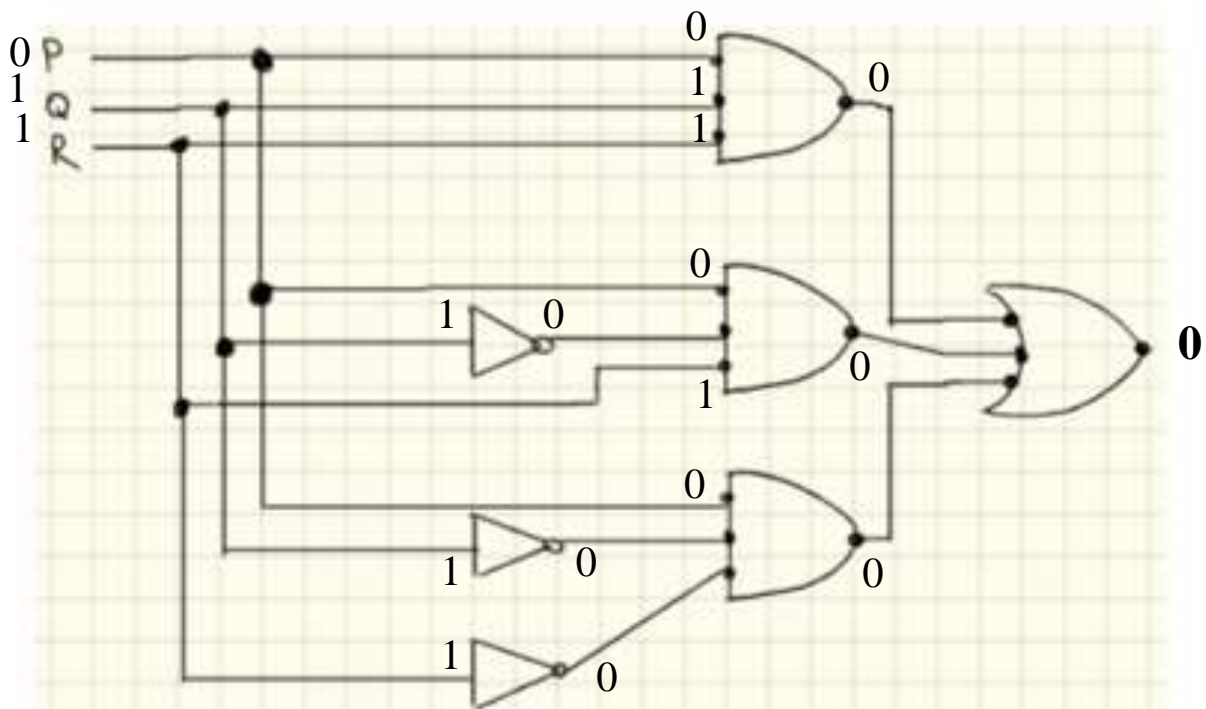

(b):

$$(P \wedge Q \wedge R) \vee (P \wedge \neg Q \wedge R) \vee (P \wedge \neg Q \wedge \neg R)$$

(c):

$$(P \wedge Q \wedge R) \vee (P \wedge \neg Q \wedge R) \vee (P \wedge \neg Q \wedge \neg R)$$

$$= P \wedge ((Q \wedge R) \vee (\neg Q \wedge R) \vee (\neg Q \wedge \neg R))$$

$$= P \wedge ((Q \wedge R) \vee (\neg Q \wedge \underbrace{(R \vee \neg R)}_{\text{True}}))$$

True

$$= P \wedge ((Q \wedge R) \vee (\neg Q \wedge \underbrace{T}_{\neg Q}))$$

$\neg Q$

$$= P \wedge ((Q \wedge R) \vee \neg Q)$$

$$= P \wedge (\underbrace{(\neg Q \vee Q)}_{\text{True}} \wedge (\neg Q \vee R))$$

True

$$= P \wedge (T \wedge (\neg Q \vee R))$$

$$= \mathbf{P \wedge (\neg Q \vee R)}$$